

## wearable computing for art

RAY LC

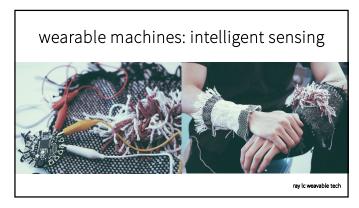


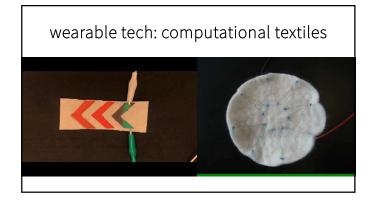







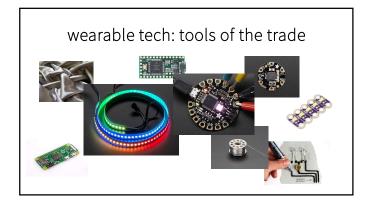

## now your turn

- connect a teensy to LEDs with resistors, and with buttons (will demo)
- instead of button to activate LED, can we use accelerometer?
- try with teensy or adafruit circuit playground (both provided)
- CONTEST: try to show an interesting and time-locked visual to your arm movement.

## wearable computing for art

RAY LC